

Team 5 Design Review

*Bucanan Howard, Daniyl Kashkan, Demetrius Van Sickle, Mohammed Alreshoud, and
Wallace McKenzie*

First Design Review with Team 2 - 8:00 pm - 9:08 pm - Meeting Notes:

- > Little to no negative feedback. PCB Traces look good. Everything looks straightforward.
- > Positive feedback on the schematic design, with inquiries about its size and potential improvements.
- > Overall comment: "Good job!"
- > Suggested to add switch main power rail.
- > Should have 1uF labeled on decoupling cap on ESP32S3.
- > Should add a note about having onboard USB on dev board.

Second Design Review with Team 7 - 9:30 pm - 10:11 pm - Meeting Notes:

- > Voltage threshold 1.2 volts.
- > Suggested labeling screen dimensions directly on the schematic for clarity and reference.
- > Suggested labeling buttons on the schematic; e.g., ☐ Adding "boxes" (label above buttons)
- > Add test points to the schematic??

Feedback for Team 5 (us) from Team 2

- GND should be labeled with 1.5 Farad (note for Bucanan).
- Label onboard USB for the PCB (also note for Bucanan).
- Overall no negative feedback, keep up the good work.
- Everything is straightforward, nothing extra or unnecessary.
- The on/off switch can be added directly to the PCB.
 - However, Daniyl will stick with designing a separate circuit for testing purposes.

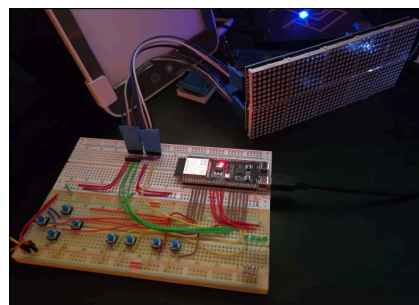
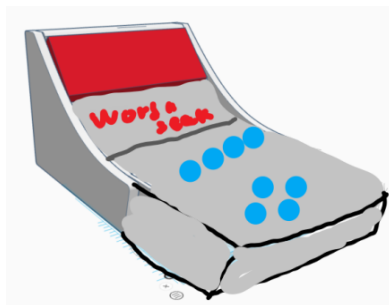


Figure 1. Figures shared by Team 5.

Feedback for Team 2 (from us to them)

- Pretty clear schematic to look at and ready.
- Specific roles defined. Every member seems caught up on the design and their own parts.
- The team also ran into plenty of problems, like proper power distribution.
 - Resolved everything properly.
- Safeguards put into place like a power-off state in case of current issues.
- OLED ground makes sense, something else Buchanan found does not.
 - Another OLED bit referenced questionably (NOT AN ISSUE).
- The battery can only be charged twice or three times.
 - Systems are put into place to check fresh batteries against garbage batteries.
- Buchanan recommended adding fuses or Zener diodes to ensure proper 12 Volt flow (??)
- Last note: the buck converter handles most of the voltage regulation.
- The fan is always on. As long as the master switch is closed, the fan is on (always).
- It takes a couple hours to charge a battery (estimated 2 hours).
 - You cannot push a battery too much while charging it, as it might break.
- Active high input. For safety, if the ESP32 fails, the active high input goes down.
 - Recommendation by Buchanan: Implement a hardware failsafe.
 - (exclusively software failsafes implemented now).
- List V_{TN} for the transistors. Rename schematic ports for clarity.
- Add a current limiting diode between VCC and sensitive components.

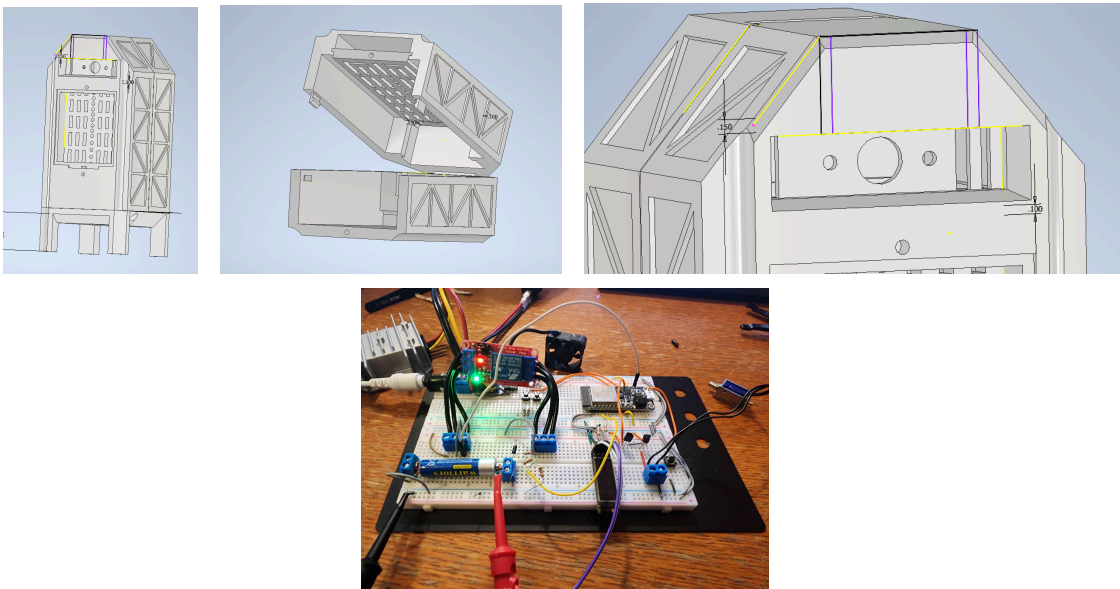


Figure 2. Figures shared by Team 2

Feedback for Team 5 (us) from Team 7

- Power distribution needs more defining.
- The threshold is 1.5V.
- Add a label above the buttons (recommended by Annika).